

SENSORS:

29/1/19

Photoresistor:

- It is like a potentiometer
- In potentiometer, we turn knob to change resistance & thereby change voltage
- In photoresistor, the ~~etc.~~ light controls the resistance in the device

More light \Rightarrow less resistance (1.5 k Ω at normal room light)

Less light \Rightarrow more resistance (10 k Ω when dark)


Usage:

- Write down the minimum and maximum resistance values for your lighting conditions.
(This will be needed for programming)

(0.3 Ω - 70 k Ω)


median ambient condition: 1.5 k Ω

Circuit

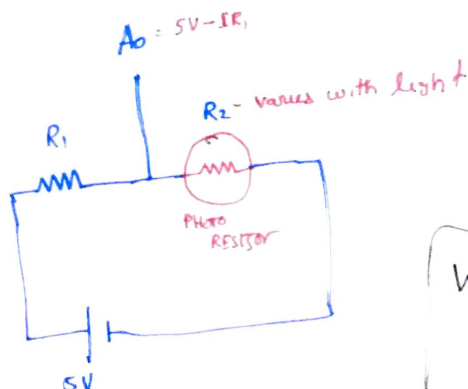

What should be our choice of R1?

Recall Voltage Divider Concept

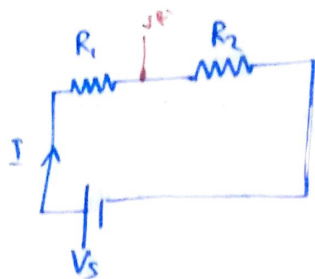

Recall Kirchhoff's Voltage law:

Algebraic sum of potential differences in any loop must be 0

$$(cc) \quad V_s + -IR_1 + IR_2 = 0$$

Potential
diff induced
by R_1

Potential
diff induced
by R_2

$$V_s = I(R_1 + R_2)$$

$$\boxed{I = \frac{V_s}{R_1 + R_2}} \rightarrow (1)$$

Now

$$V_{R_1} = IR_1$$

Sub I from (1)

$$\boxed{V_{R_1} = \left(\frac{V_s}{R_1 + R_2} \right) R_1}$$

By varying R_2 , we can vary the voltage across V_{R_1}

This is the key concept behind potentiometer
* photo resistors

Choice of R_1 for photo resistor circuit


- At ambient temp, let us have ofp Analog Voltage to be 2.5 V (mid value)
- At ambient temp, Resistance by photo resistor $R_2 = 1.3 \text{ k}\Omega$

Then

$$V_{\text{out}} = \left(\frac{V_{\text{in}}}{R_1 + R_2} \right) R_1 = \frac{5}{1.3 + R_1} \cdot 1.3 = 2.5$$

$$\Rightarrow \boxed{R_1 = 1.3 \text{ k}\Omega}$$

Circuit

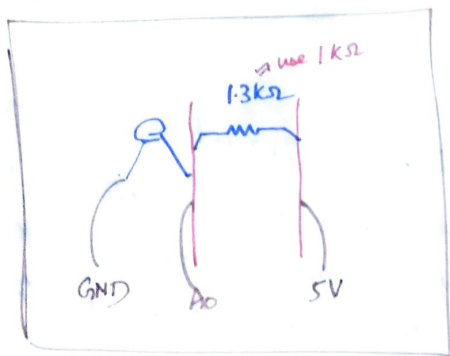

- A_0 value $\in (0, 1023)$


- When Ambient V_0 is $5/2$ (at mid port)
We should see ambient $A_0 \approx 500$

App 100

UV Sensor

Arduino S12 D

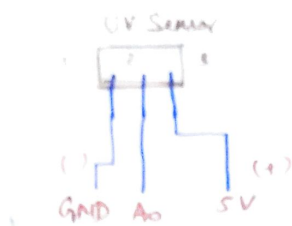- * It is an analog sensor on a Break out board
- * (ie) the output of sensor is read from the analog pin.




Breakout boards

- * Another Integrated Circuit which can be attached to Arduino.
- * Breakout implies, they are not specific to Arduino boards, but can be used with other boards too (con like shields)

Pull up / pull-down resistor : When a circuit is not closed (like open switch, other EM waves can interact & change the state). To prevent that we use pull-up / pull-down Resistor


Pull-up : (Resistor to V_{cc})

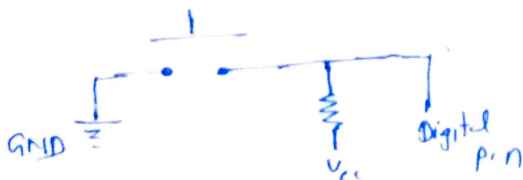

SWITCH OFF : PIN IS HIGH

SWITCH ON : PIN IS LOW


PULL DOWN

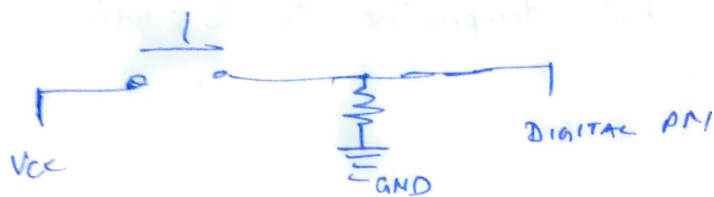

SWITCH OFF : PIN IS LOW
SWITCH ON : PIN IS HIGH

Digital

Temperature & Humidity Sensor

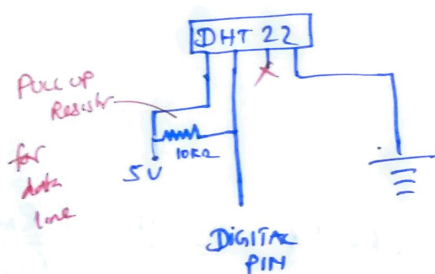


• To use this sensor, use the DHT library

- The output from a digital sensor is read through variations in digital signals
- These variations in digital pins are captured with external libraries from manufacturers

Thermistor (Analog device, same as photo resistor
but temperature controls resistance)

Thermist

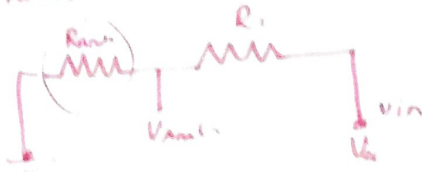

Computing Resistance from analog value 0-1023

$$V_{Analog} = \frac{V_{cc}}{1023} \times A_0 \quad V_{cc} = 5V \rightarrow (1)$$

From voltage divider eqn.

$$V_{analog} = \frac{V_{cc} \cdot R_{analog}}{R_1 + R_{analog}} \rightarrow (2)$$

Sub (2) in (1)

$$A_0 = \frac{1023 \cdot \frac{V_{cc} \cdot R_{analog}}{R_1 + R_{analog}}}{\frac{V_{cc} \cdot R_{analog}}{R_1 + R_{analog}}} = 1023 \left(\frac{R_{analog}}{R_1 + R_{analog}} \right)$$

$$\Rightarrow \boxed{R_{analog} = \frac{R_1}{\left(\frac{1023}{A_0} - 1 \right)}}$$